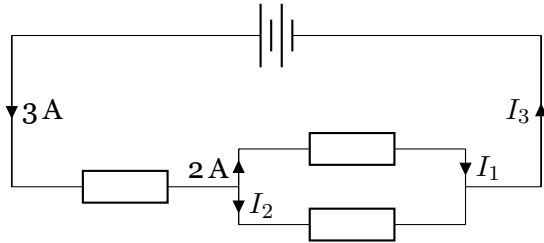



Solving Circuits Part 1

1. In each of the questions below use Kirchoff's Laws to calculate the missing currents and potential differences.


(a)




(b)

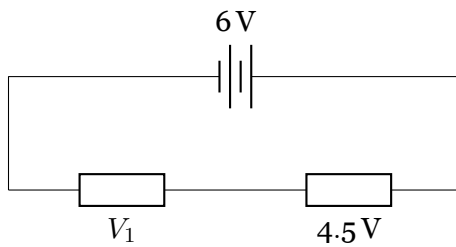


(c)

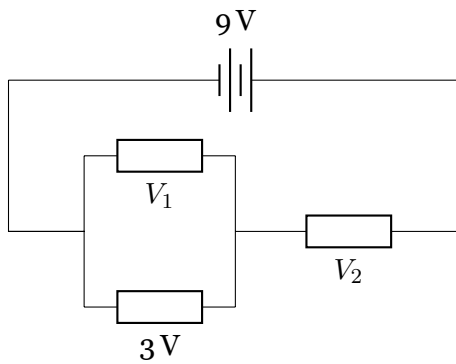

(d)

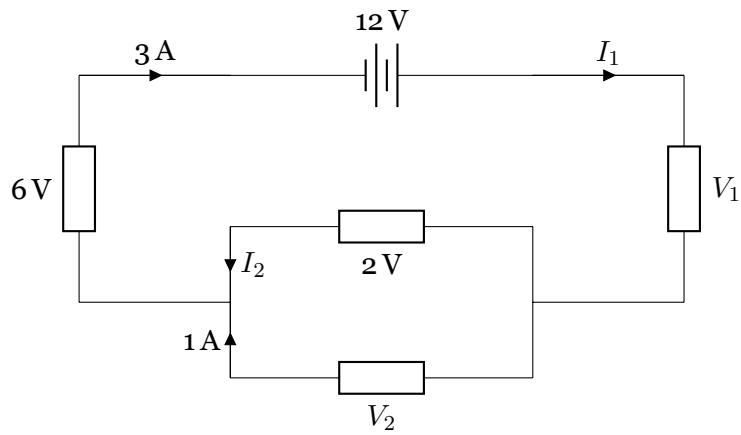

(e)

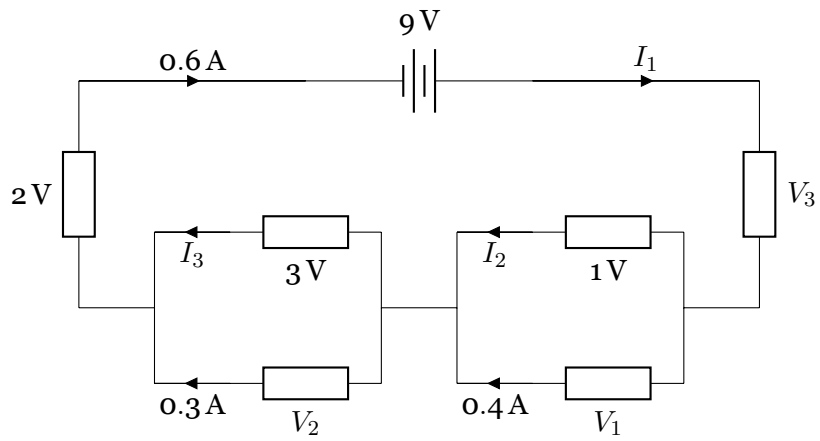


(f) *If you have finished...* Calculate the resistance of the individual resistors in (e) above and the effective resistance of the whole circuit.


Solving Circuits Part 2

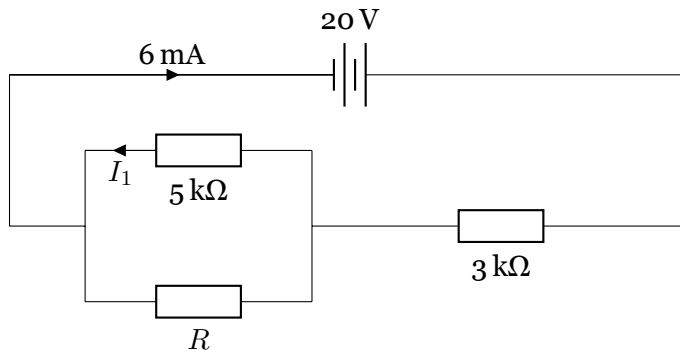2. In the circuit below, calculate:


- the p.d. across the $3\text{ k}\Omega$ resistor;
- the current through the $5\text{ k}\Omega$ resistor;
- the resistance of resistor R .



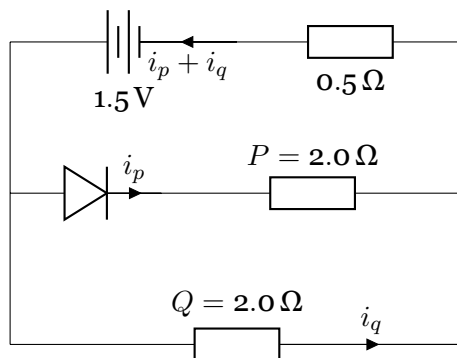
3. The circuit below includes a silicon diode which has a constant p.d. across it of 0.6 V . Calculate the current through resistors P and Q and the cell current.



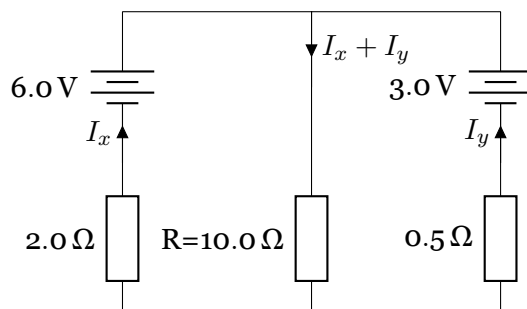
4. Calculate the current through and potential difference across resistor R .



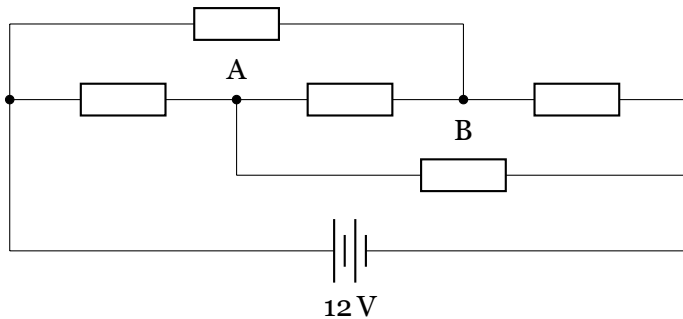5. Five resistors having the same resistance, $100\ \Omega$, are connected as shown in the circuit below. A battery of 12 V and negligible internal resistance is connected across the circuit.



- By considering the arrangement of resistors, determine the potential difference between the points A and B.
 - Determine the current flowing through each of the resistors and the current through the battery.
6. A transmission line can be represented by a chain of resistors. Such a chain has elements which consist of two $3\ \Omega$ resistors. These elements are connected to form the chain as shown in the diagram.

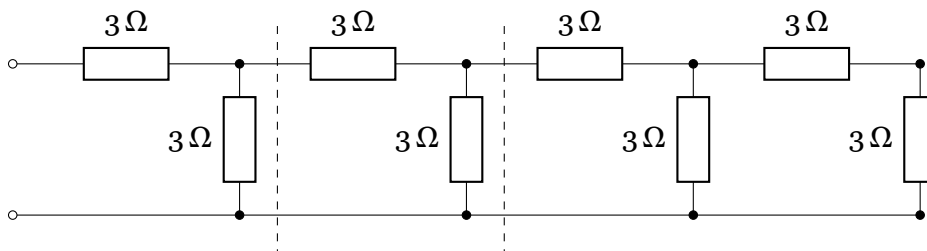

- Calculate the resistance between the terminals of such a chain which consists of:
 - 2 elements only (i.e. 4 resistors);
 - 3 elements only (i.e. 6 resistors);
- By calculating the resistance of an infinitely long chain of resistors, show that adding more elements to a chain which is already 3 elements long produces negligible change in resistance.